

Problem Set – 1

CS 230, Spring 2023

Questions

- Which of the following are true regarding XOR (\oplus) operation if $A_1 \oplus A_2 \oplus A_3 = P$?
 - $A_1 \oplus A_2 \oplus P = A_3$
 - $A_2 \oplus A_3 \oplus P = A_1$
 - $A_1 \oplus A_2 = A_3 \oplus P$
 - $A_1 \oplus A_2 \oplus A_3 \oplus A_4 = P$
- The minimum number of 2-input NOR gates required to implement the function is __
$$f = \overline{\overline{A} + [B + \overline{C}(AB + AC)]}$$
- The minimum number of 2-input NOR gates required to implement a 4-variable function represented in the form of minterms as, $f = \sum(0,2,5,7,8,10,13,15)$ is?
- Minimum how many 2-input NAND gates are required to implement the Boolean function $f = (A + C)(B + D)$?
- A function f^d is said to be dual function of f if all the OR operations in f are changed to AND in f^d and all the AND operations are changed into OR respectively.
 f is an orthogonal function if dual of f and complement of f are same. [$f^d = f^c$]
In a system of n literals, how many such orthogonal functions are possible?
- If $M = \overline{XYZ} + \overline{X}\overline{Y} + YZ$ then dual and compliment of M are respectively,
 - $(XYZ + \overline{X}\overline{Y}) \cdot (Y + Z)$ and $[(\overline{X} + \overline{Y} + \overline{Z}) + (\overline{X} + \overline{Y})] \cdot YZ$
 - $[(X + Y + Z + \overline{X} \cdot \overline{Y})] \cdot \overline{YZ}$ and $[XYZ + (\overline{X} + \overline{Y})] \cdot \overline{YZ}$
 - $[(\overline{X} + \overline{Y} + \overline{Z}) + (\overline{X} + \overline{Y})] \cdot (Y + Z)$ and $(XYZ + \overline{X}\overline{Y}) \cdot \overline{YZ}$
 - $[\overline{XYZ} + \overline{X} + \overline{Y}] \cdot \overline{YZ}$ and $[(X + Y + Z) + \overline{X} \cdot \overline{Y}] \cdot YZ$
- There exists a Boolean function $f(a, b, c, d)$ such that,
$$f(a, 0, 0, d) = 1$$
$$f(1, b, 1, d) = b + d$$
$$f(a, 1, c, d) = ad + c$$

How many literals are there in minimum SOP expression of f ?

8. Consider the following K-map.

		AB			
		00	01	11	10
CD	00	1	1		1
	01	X			
	11	X			
	10	1	1		X

Here X denotes “don’t care” term. Which means, the outcome of the function is not influenced by the value being 0 or 1. What is the minimal form of the function represented by above K-map?