

# Problem Set – 2 Solutions


CS 230, Spring 2023

## Questions

1. Consider a full-binary subtractor that accepts three input bits  $a$ ,  $b$ , and  $B_{in}$ , and outputs  $c$  and  $B_{out}$ .  $a$  and  $b$  are the operands for the subtraction operation and  $B_{in}$  is the borrow taken by the previous digit.  $c$  is the resulting bit for the operation  $(a - b)$  and  $B_{out}$  is the borrow taken from the next digit for the subtraction. Then the boolean expression for  $c$  and  $B_{out}$  is:

- a.  $c = \bar{a} \oplus b \oplus B_{in}$ ;  $B_{out} = \bar{a}B_{in} + a\bar{b} + bB_{in}$
- b.  $c = a \oplus \bar{b} \oplus B_{in}$ ;  $B_{out} = \bar{a}B_{in} + \bar{a}b + bB_{in}$
- c.  $c = a \oplus b \oplus B_{in}$ ;  $B_{out} = \bar{a}B_{in} + \bar{a}b + bB_{in}$
- d.  $c = a \oplus b \oplus B_{in}$ ;  $B_{out} = \bar{a}B_{in} + \bar{a}b + b\bar{B}_{in}$

A full subtractor will look like this:

 

Truth Table of Full Subtractor:

$a$	$b$	$B_{in}$	$c$	$B_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Solving for  $c$


$$\begin{aligned}
 c &= \bar{a}\bar{b}B_{in} + \bar{a}b\bar{B}_{in} + a\bar{b}\bar{B}_{in} + abB_{in} \\
 &= B_{in}(ab + \bar{a}\bar{b}) + \bar{B}_{in}(a\bar{b} + \bar{a}b) \\
 &= B_{in}(\overline{a \oplus b}) + \bar{B}_{in}(a \oplus b) \\
 &= a \oplus b \oplus B_{in}
 \end{aligned}$$

Solving for  $B_{out}$  using K-map.

$a \backslash b, B_{out}$	00	01	11	10
0	0 <sub>0</sub>	1 <sub>1</sub>	1 <sub>3</sub>	1 <sub>2</sub>
1	0 <sub>4</sub>	0 <sub>5</sub>	1 <sub>7</sub>	0 <sub>6</sub>

$$B_{out} = \bar{a}B_{in} + \bar{a}b + bB_{in}$$

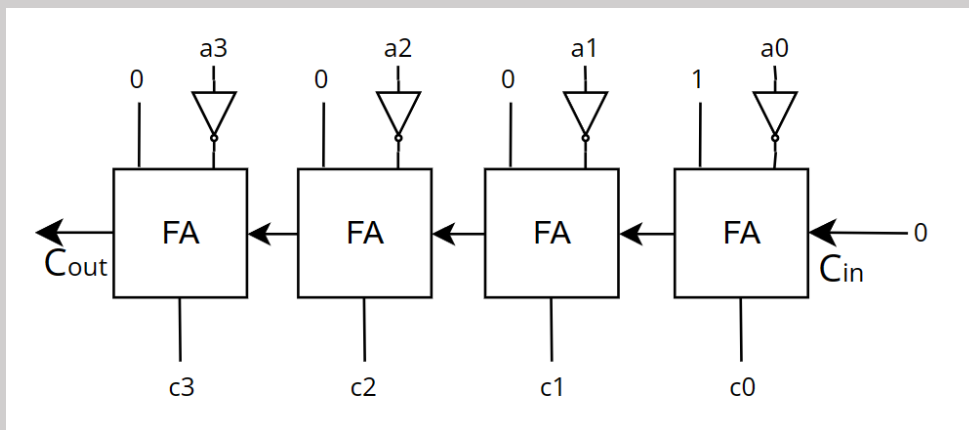2. Consider the following logic circuit. Suppose binary numbers are represented in 2's complement form.



- What is the output  $C = c_3c_2c_1c_0$  for input  $A = 0101$ ?
- What does the above circuit do?
  - Outputs  $A + 1$
  - Outputs  $\bar{A}$
  - Outputs  $-A$
  - Outputs  $-A + 1$

a. It is 4 bit adder in which one operand is fixed 0001 and the second operand is  $\bar{A}$

We have  $A = 0101$

$$\bar{A} = 1010$$


$$C = \bar{A} + 0001$$

$$= 1010 + 0001$$

$$= \mathbf{1011}$$

b. The output of the circuit is  $\bar{A} + 1$ , which represents  $-A$  in 2's complement form.

 3. You have to design a two bit greater than comparator logic circuit ( $A > B$ ). Following incomplete circuit is provided to you. Name appropriate logic gate for each red box to complete the circuit.



The truth table for the comparator:

$A_1$	$A_0$	$B_1$	$B_0$	$C$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Solving using K-map


$A_1, A_0 \backslash B_1, B_0$	00	01	11	10
00	0 0	0 1	0 3	0 2
01	1 4	0 5	0 7	0 6
11	1 12	1 13	0 15	1 14
10	1 8	1 9	0 11	0 10

$$C = A_0 \overline{B_1} \overline{B_0} + A_1 A_0 \overline{B_0} + A_1 \overline{B_1}$$

$$= (A_1 + \overline{B_1}) A_0 \overline{B_0} + A_1 \overline{B_1}$$

Mapping the expression with circuit:

 
- I) AND Gate
- II) OR Gate
- III) AND Gate
- IV) OR Gate



4. A toggle flip-flop (T flip-flop) toggles its output when the input  $T = 1$  during clock signal transition. For input  $T = 0$ , the output remains same. The state table of T flip-flop is as follows:


T	$Q_n$	$Q_{n+1}$	
0	0	0	Unchanged/hold
0	1	1	Unchanged/hold
1	0	1	Toggle
1	1	0	Toggle

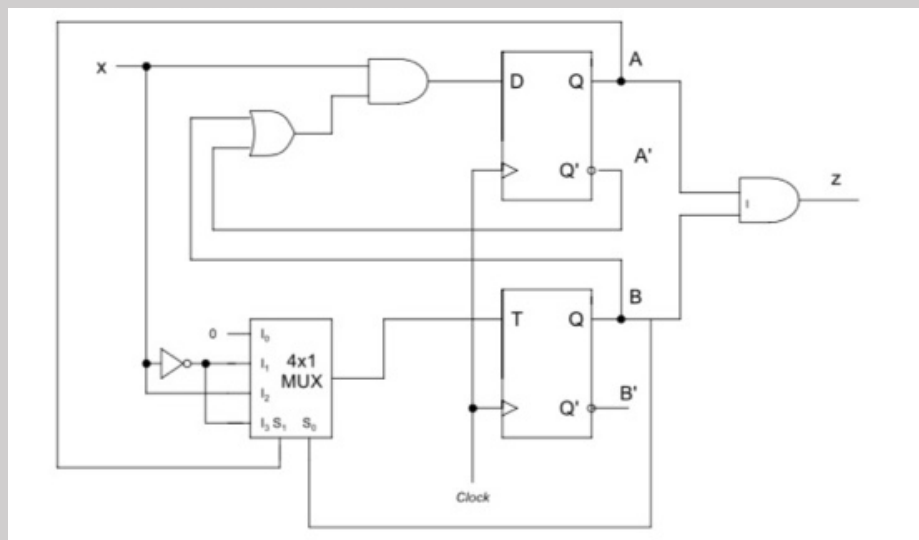Complete the state table of the following circuit.



Current State		Input	Next State		Output
A	B	x	A	B	z
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	1	1	1

 5. You have to design a 2 bit mod 3 binary counter using D flip-flops. The counter should follow the following sequence:  
 0, 1, 2, 0, 1, 2, 0.....  
 You are given the following circuit.



Write the Boolean expression for  $D_A$  and  $D_B$  in terms of  $Q_A$ ,  $\overline{Q_A}$ ,  $Q_B$  and  $\overline{Q_B}$  to complete the circuit.

The state table will be:

$Q_A$	$Q_B$	$Q_{A+1}$	$Q_{B+1}$	$D_A$	$D_B$
0	0	0	1	0	1
0	1	1	0	1	0
1	0	0	0	0	0
1	1	X	X	X	X

K-map for  $D_A$

$Q_A \backslash Q_B$	0	1
0	0	1
1	0	-

$$D_A = Q_B$$

K-map for  $D_B$

$Q_a \backslash Q_b$	0	1
0	1 0	0 1
1	0 2	- 3

$$D_B = \overline{Q_A} \overline{Q_B}$$

6. What is the minimum number of D flip-flops to design a counter for the sequence 0, 0, 1, 1, 2, 2, 3, 3, 4, 4, 5, 5, 6, 6, 7, 7, 0, 0, 1, 1...?

Since each number is repeated two times, we can assign two different states to each number. The sequence then can be written as: 0<sub>1</sub>, 0<sub>2</sub>, 1<sub>1</sub>, 1<sub>2</sub>, 2<sub>1</sub>, 2<sub>2</sub>, 3<sub>1</sub>, 3<sub>2</sub>, 4<sub>1</sub>, 4<sub>2</sub>, 5<sub>1</sub>, 5<sub>2</sub>, 6<sub>1</sub>, 6<sub>2</sub>, 7<sub>1</sub>, 7<sub>2</sub>, 0<sub>1</sub>, 0<sub>2</sub>....

We have 16 distinct states.

To represent  $m$  distinct states, we need a minimum of  $\lceil \log_2(m) \rceil$  flip-flops, because each flip-flop can toggle between two states.

So, for 16 states, you need **4 flip-flops**.